


坂井グループ： 形式的検証とテスト段階の修復

論理設計デバッグ時の自動修正技術

藤田昌宏

Debugging process

 
- Given counter examples (test cases that do not produce correct outputs), do the followings:
 - Locate suspicious portions of HW/SW (**Diagnose**)
 - Come up with possible **corrections** on them
 - Make sure the corrected HW/SW is OK (**start verification process again**). If not, repeat the debugging process



On Nu **Let's discuss diagnosis (existing techniques) first** ging

Basic Simulation-based Diagnosis (1)


Path tracing

 

Basic Simulation-based Diagnosis (2)

Path tracing

 Most suspicious portions

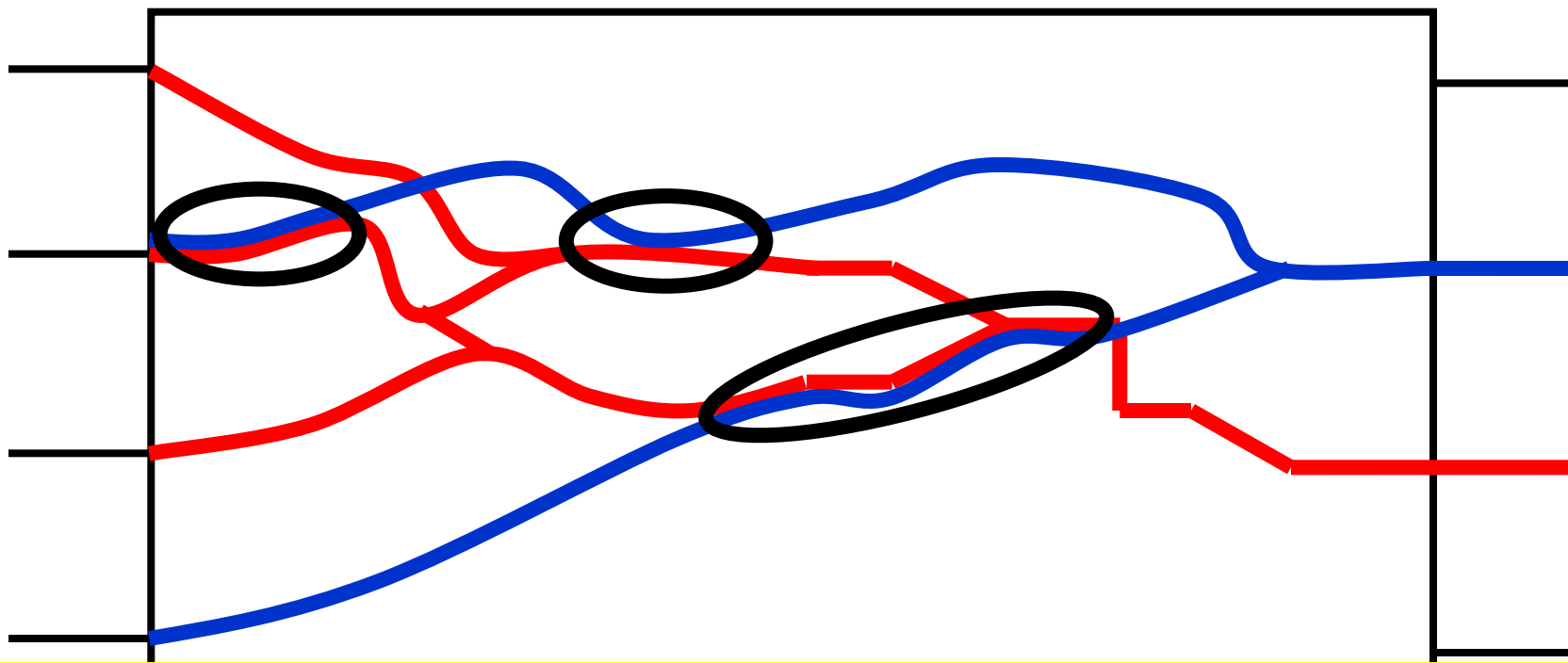


This can be easily formulated as SAT problem

What can we do with SAT-based debugging method ?


- It shows a set of internal signals:
 - By modifying those portions of circuits using all of primary inputs, entire design may become correct
 - Or may not, since we do not know complete specification
 - Only counter examples are given

 It only suggests where to modify, not the way to modify and also can be incomplete




Debug: Sampling based synthesis with refinement

 - Formal verifier (SAT solvers) can generate counter examples, if specification is given **formally**
- Hopefully, numbers of iteration are small
- First fix suspicious portions (**discovered by SAT-based**)



Correction method

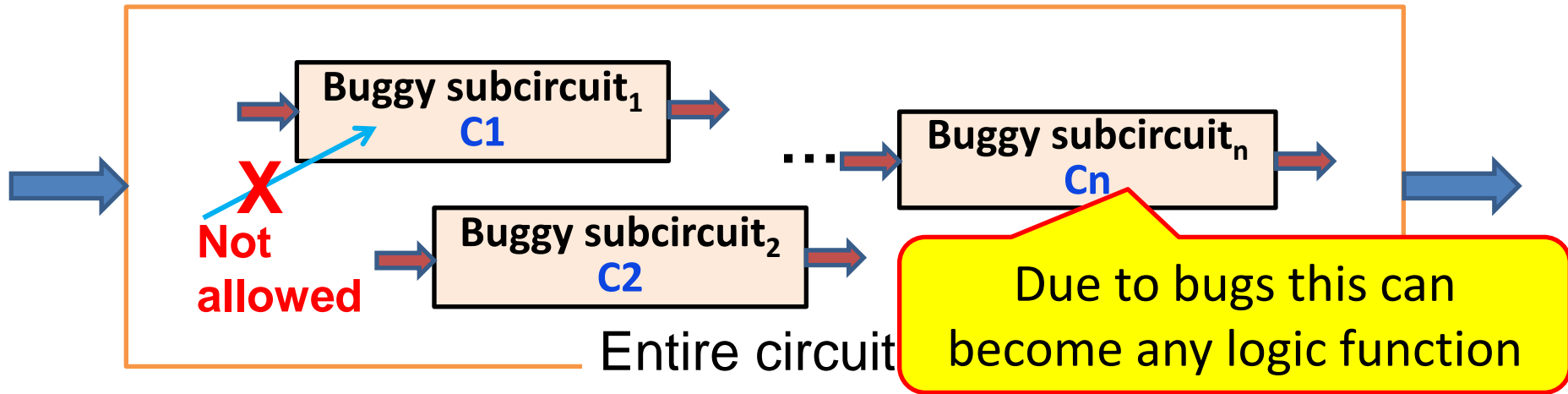- Bugs exist only **inside suspicious subcircuits**
- They cannot refer to signals outside of the subcircuits
- **Multiple bugs are targeted**



- **Buggy subcircuits** should be modified in such a way that **entire circuit becomes correct**
- We do not know those functions, but we know the inputs
 - **Use Look Up Table (LUT) for each of subcircuit**

Problem formulation

- Look up Table (LUT) can represent all logic functions with the set of inputs
 - Introducing **programmable variables**
- Then the problem becomes QBF (Quantified Boolean Formula)

$\exists \text{ProgVar. } \forall \text{Input. } f(\text{ProgVar}, \text{Input}) =$

Target $\wedge \text{SPEC}(\text{Input})$ programming of LUT, the circuit is
 eq to the spec

Solve the problem with repeated application
 of SAT solvers
 (actually Incremental SAT solvers)

The problem can be efficiently solved by “incremental” SAT solvers

Performance in practice:

10,000 gates, 100 multiple errors need
only a couple of minutes and tens of iterations !

Set of generated counter examples (x_1, x_2, \dots, x_n) :
Complete test vectors (100% verification) assuming
bugs are only inside subcircuits

$\dots \wedge f(Y, x_{n-1}) = Spec(x_{n-1}) \Rightarrow \text{SAT, SOLUTION IS } (y_n, x_n)$


$\exists Y.X. f(Y, X) \neq Spec(X) \wedge f(Y, x_1) = Spec(x_1) \wedge f(Y, x_2) = Spec(x_2)$

$\dots \wedge f(Y, x_{n-1}) = Spec(x_{n-1}) \wedge f(Y, x_n) = Spec(x_n) \Rightarrow \text{UNSAT}$

- There are no more counter examples, as long as it works correctly under inputs (x_1, x_2, \dots, x_n)



バグ修正のフロー

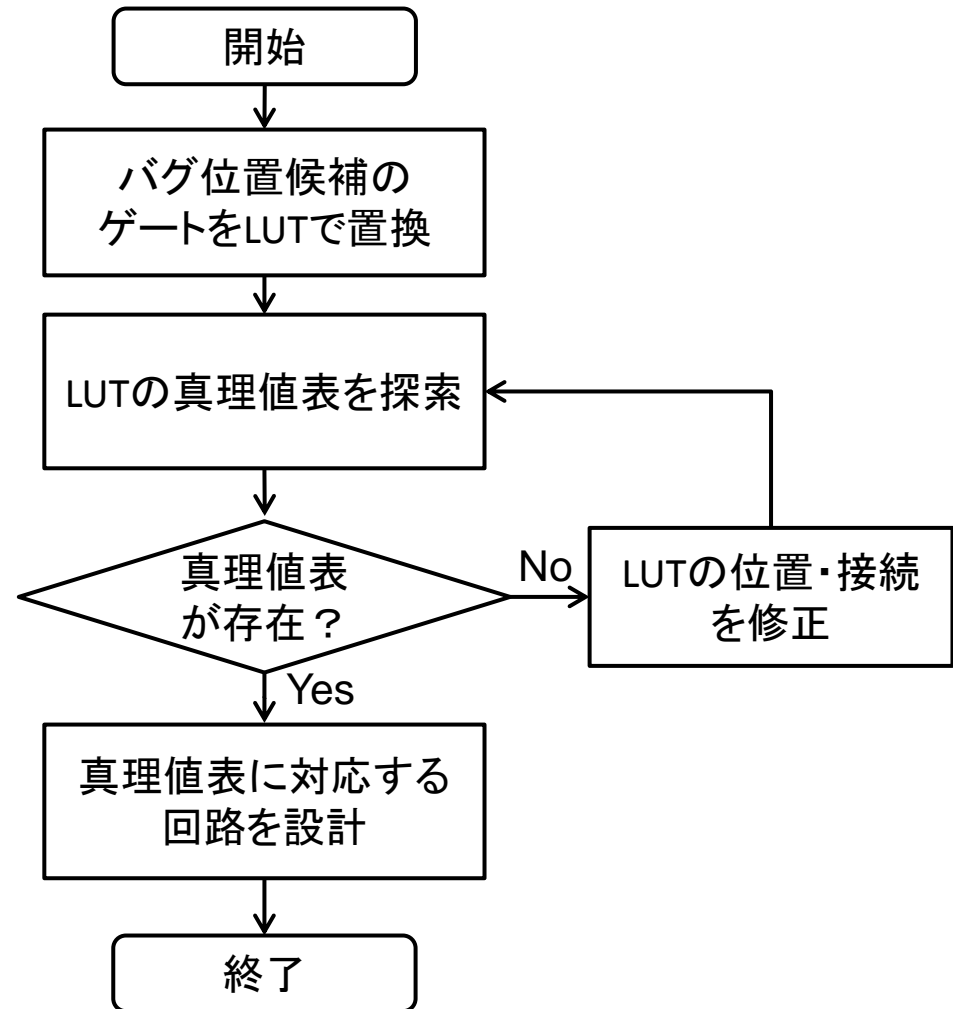- バグ位置の候補をLUTで置換
- 設計を仕様と等価にするLUTの真理値表を探索
- 真理値表が求まった場合: 真理値表に従って設計を修正する
- デバッグ可能な場合には、短時間にいつも解が見つけられる
- 真理値表が見つからない場合:
LUTの配置や変数の接続を修正する必要がある




LUTを用いたバグ修正の問題点

  - 変数の不足によるバグを修正できない:変数を追加する
- 回路中の変数は多数ある
:効率よく探索する手法が必要




LUTが変数 c を入力に持っていないため、設計を仕様と等価にすることができない

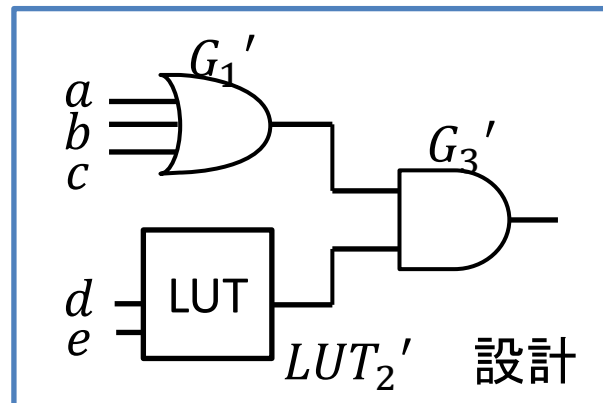


変数値の絞り込み

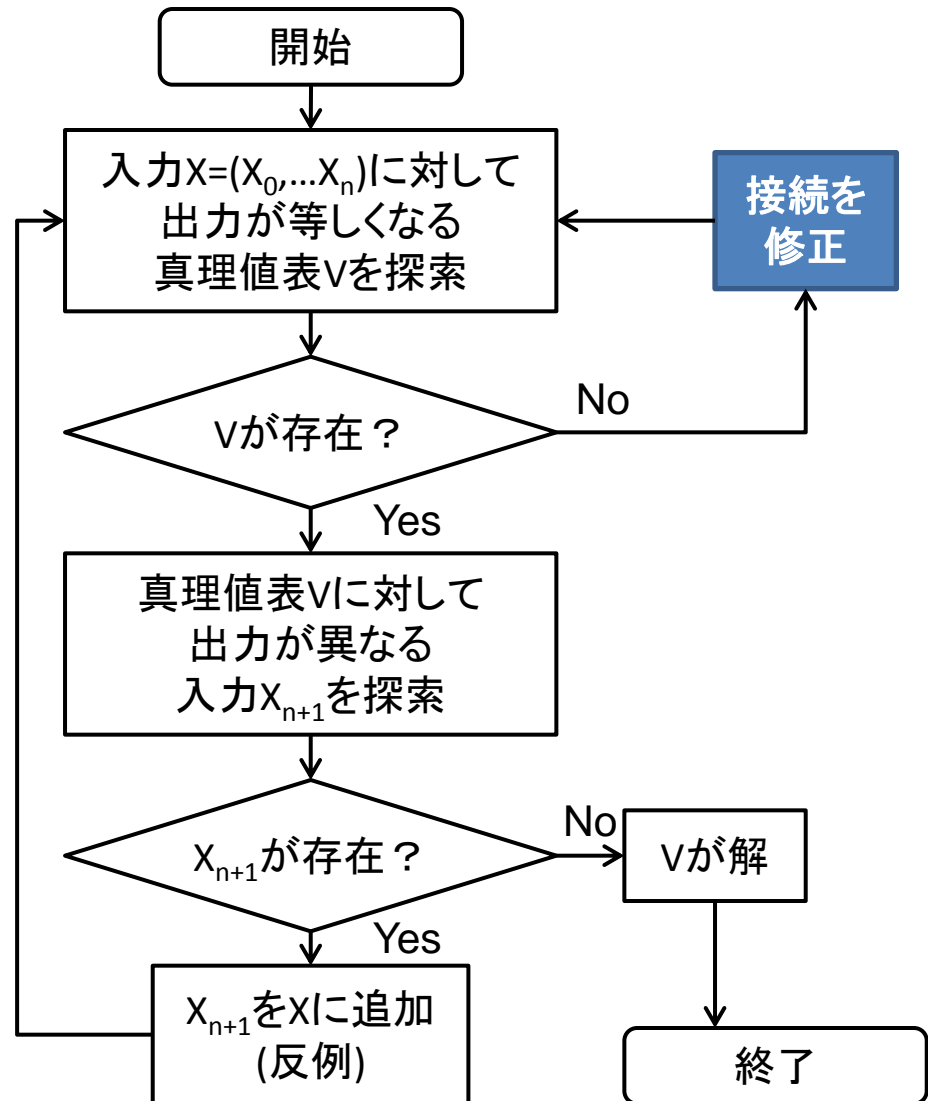- LUTに追加する変数を絞り込む
 - 仮定:
設計中のLUTは1つ
(複数のLUTがあり、
いかなるLUTの出力値も
他のLUTの入力値に伝搬
しない場合に拡張可能)
 - バグを修正できない場合:
入力パタンの集合 X
(反例の集合)に
次のスライドで示す
条件を満たすものが
含まれる




変数値の絞り込み: 修正不可能な場合

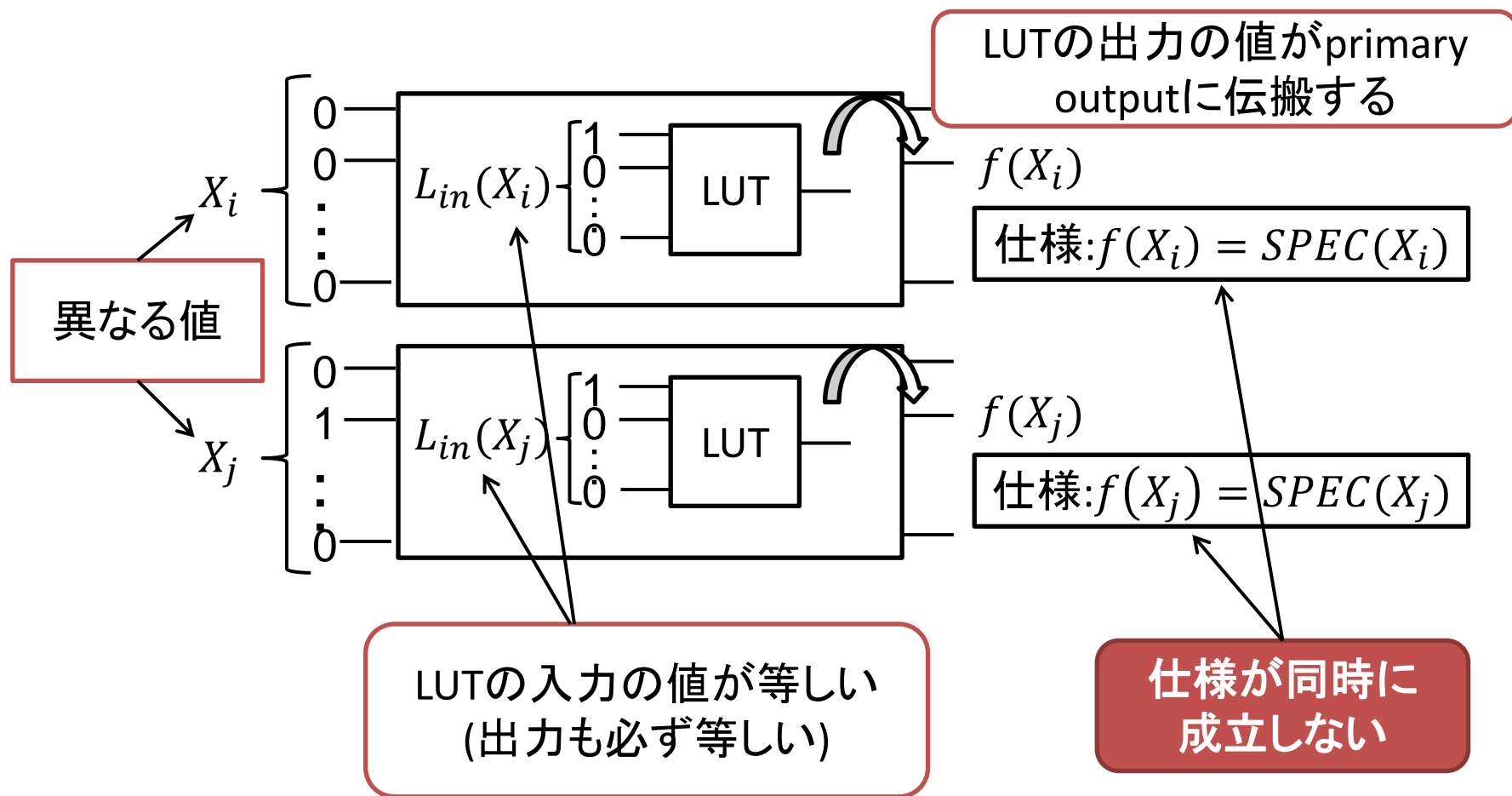- 入力値 X_i, X_j が以下の条件を満たすとき、いかなるLUTの真理値表の割り当てによっても修正不可能




変数値の絞り込み: 追加される変数の必要条件

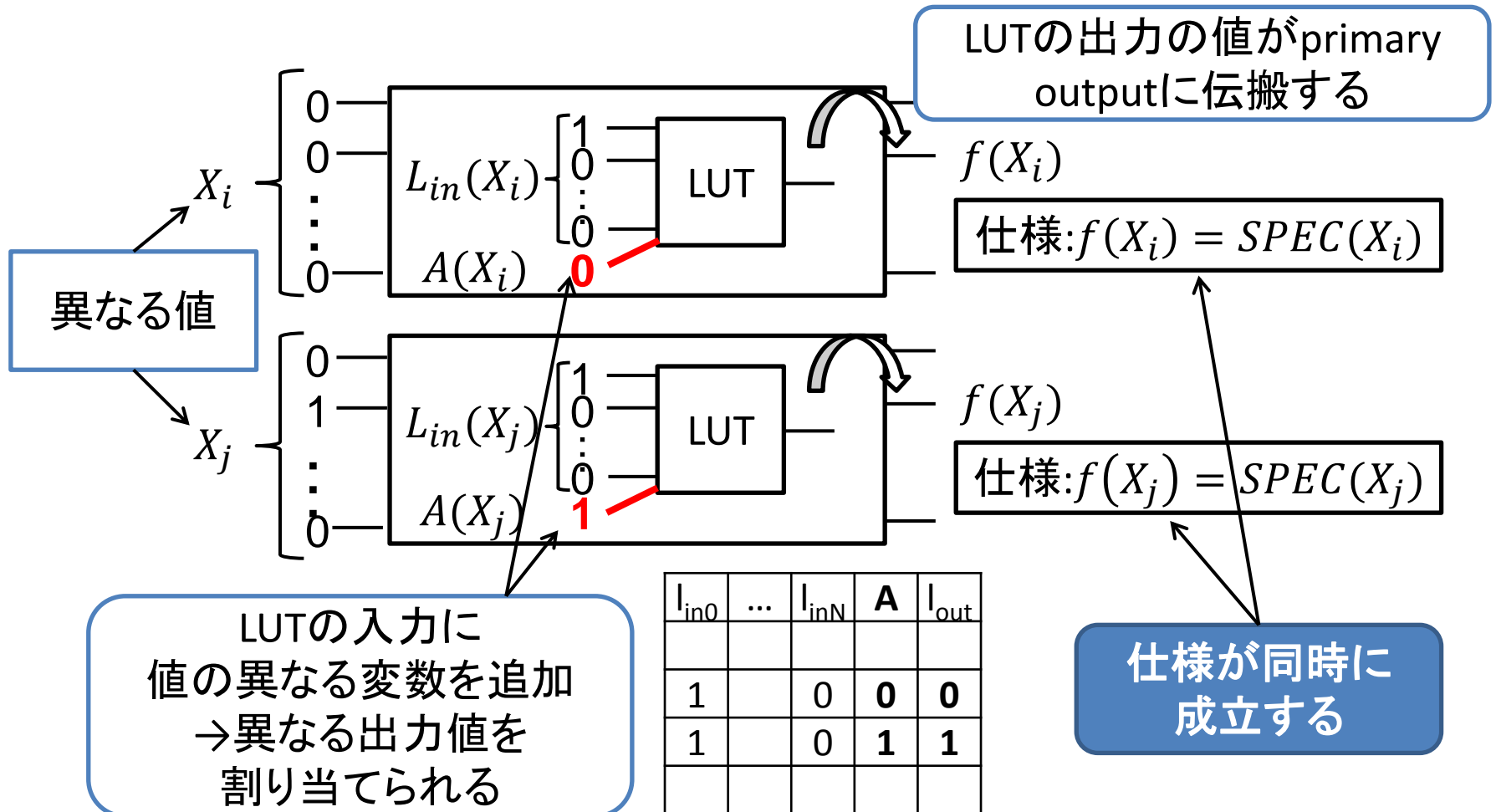- バグを修正するために追加すべき変数:
 入力 X_i, X_j に対して以下の条件を満たす必要がある



マルチプレクサを利用した探索の効率化

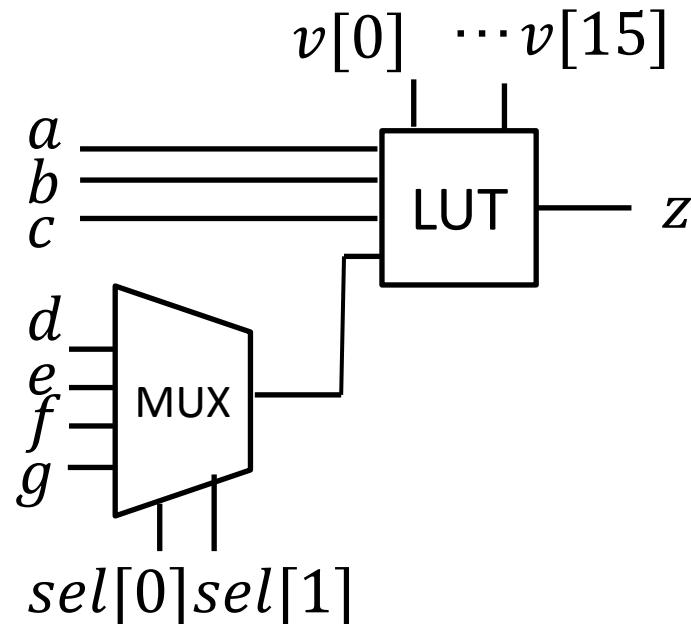- マルチプレクサを利用して複数の変数を追加
- 複数の変数について同時に探索可能
- LUTに比べて変数が少なく、効率が良い



論理設計のデバッグ

- 論理回路の1つのゲートをLUTで置き換え
 - 3入力のゲートを置き換え
- LUTの1つの入力を取り除く
- 変数の追加によって設計を仕様と等価にできるかを調べる
- 例題: ISCAS85 ベンチマーク
- 実験環境
 - OS: Linux CPU: Intel Xeon 2.66GHz Memory: 20GB
 - SATソルバ: PicoSAT
 - Verilog→CNFの変換: ABC, AIGER

論理設計のデバッグの結果

- すべての設計が仕様と等価に
- 設計中の変数のうち10%~40%が候補に
- MUXにより時間が80%以上短縮

PI: 回路の入力から追加
Filtering: 変数の絞り込み
Filtering+MUX:
マルチプレクサを利用

回路	変数	手法	成功/ 回路数	候補数	割合	繰り返し	時間 [sec]
c499	243	PI	0/5	N/A	N/A	18.8	46.4
		Filtering	5/5	88.6	36%	14.0	48.3
		Filtering+MUX	5/5	88.6	36%	16.4	2.3
c880	443	PI	1/5	61.0	14%	55.0	80.8
		Filtering	5/5	54.2	12%	10.6	57.0
		Filtering+MUX	5/5	54.2	12%	11.6	2.6
c1355	587	PI	0/5	N/A	N/A	12.0	60.6
		Filtering	5/5	155.8	27%	13.0	227.7
		Filtering+MUX	5/5	155.8	27%	19.6	3.3

論理設計のデバッグの結果

回路	変数	手法	成功/回路数	候補数	割合	繰り返し	時間[sec]
c1908	911	PI	2/5	34.0	4%	119.6	69.2
		Filtering	5/5	194.2	21%	14.0	284.5
		Filter+MUX	5/5	194.2	21%	17.0	3.9
c2670	1194	PI	0/5	N/A	N/A	6.8	708.1
		Filtering	5/5	142.2	12%	12.8	83.2
		Filter+MUX	5/5	142.2	12%	22.4	4.7
c3540	1670	PI	0/5	N/A	N/A	45.2	154.9
		Filtering	5/5	503.8	30%	11.4	915.9
		Filter+MUX	5/5	503.8	30%	20.0	7.8
c5315	2476	PI	0/5	N/A	N/A	30.8	915.5
		Filtering	5/5	324.6	13%	9.8	268.1
		Filter+MUX	5/5	324.6	13%	13.6	8.8
c7552	3604	PI	0/5	N/A	N/A	5.4	1484.3
		Filtering	5/5	1016.0	28%	9.8	3990.1
		Filter+MUX	5/5	1016.0	28%	16.6	15.9

実設計のデバッグ

- 例題: コントローラ回路のRTL設計
 - 実際の設計で行われた変更をバグとする
- 合成された論理回路に対し手法を適用
- 順序回路を3サイクル分の組み合わせ回路に展開
- デバッグに成功
 - 提案手法により探索時間が短縮された

回路	セル数	変数数	手法	候補数	時間[sec]
Industrial	8289	3209	PI	395	>5h
			Filtering	100	972.3
			Filtering+MUX	100	172.5

RTL設計のデバッグ

- RTL設計に対する性能を評価
- 例題: ARM Cortex Microprocessor
- RTL設計にバグを挿入

バグの種類	仕様	バグ
論理の誤り	$A = B \& C$	$A = B \mid C$
余剰な変数	$A = B \& C$	$A = B \& C \& D$
変数の誤り	$A = B \& C$	$A = B \& D$
変数の不足	$A = B \& C$	$A = B$

- Synopsys Inc. Design Compiler を用いて合成
- Synopsys Inc. Formality によりバグ位置の候補を特定

RTL設計のデバッグ

- 例題: ARM Cortex Microprocessor
 - FFを取り除く
 - FFの出力を回路のprimary input、FFへの入力を回路のprimary outputとして等価性検証
 - 入力: 895 出力: 923 セル数: 9,545 変数数: 10,500
- 実験環境
 - OS: Linux CPU: Intel Xeon 2.66GHz Memory: 20GB
 - SATソルバ: MiniSat
 - Verilog→CNFの変換: ABC, AIGER


RTL設計のデバッグの結果

- バグの種類によって異なる結果
 - 余剰な変数のバグにおいて多くの場合成功
 - その他のバグは3~4個の例題について成功


バグ	成功/ 回路数	変数の 追加	候補数	割合	ループ	時間[sec]	
						成功時	失敗時
論理の誤り	3/10	0	N/A	N/A	10.4	29563.1	213.8
余剰な変数	9/10	0	N/A	N/A	14.1	38141.4	1550.2
変数の誤り	3/10	3	4287.7	40%	13.0	39192.1	173.2
変数の不足	4/10	4	5333.8	50%	39.0	38016.6	480.2

考察: デバッグが行えない場合(1)

- ゲートの順番によりデバッグ不可能な場合がある

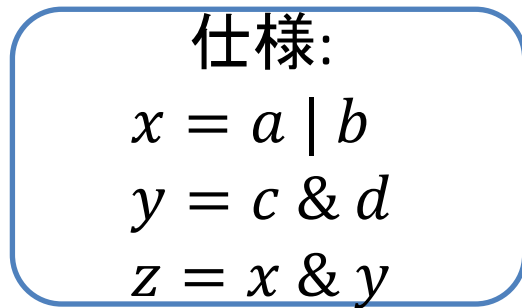

バグを挿入

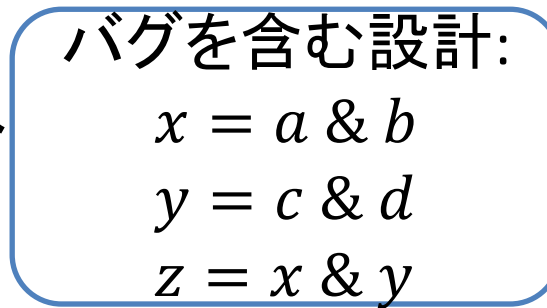


合成




合成

仕様を実現する論理回路

 


合成結果

 


ゲートをLUTで置き換えても仕様を実現できない

考察: デバッグが行えない場合(2)


- 変数が存在しない場合がある

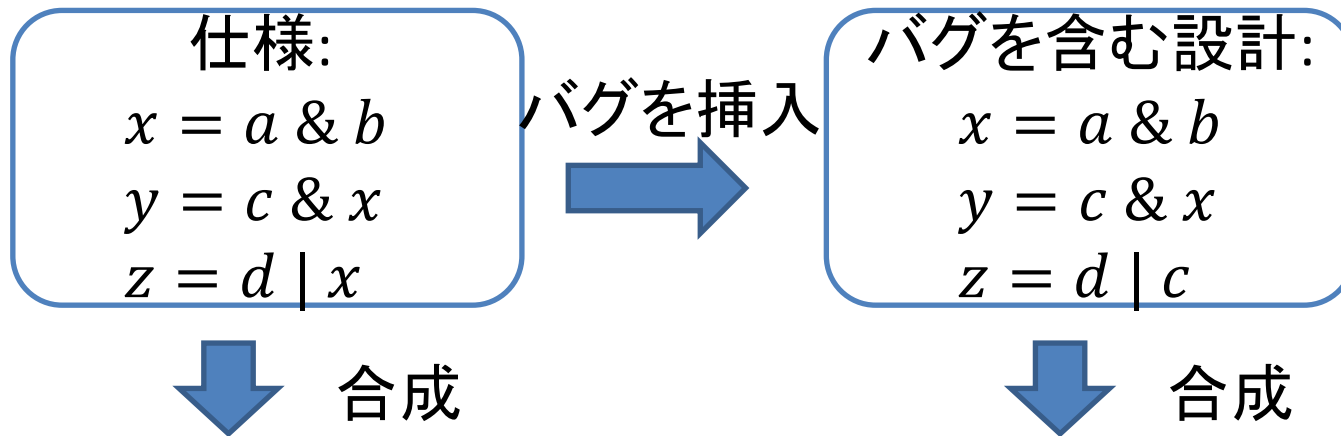

仕様を実現する論理回路

 

合成結果

 

追加すべき
変数が
存在しない

今後の課題

- 接続順の入れ替えとLUTの拡大
 - より多くのバグに対応
 - 計算量は増加する
- 複数の変数を追加
 - 3つ以上の反例から絞り込みを行う
- LUT以外の回路を用いた計算量の削減